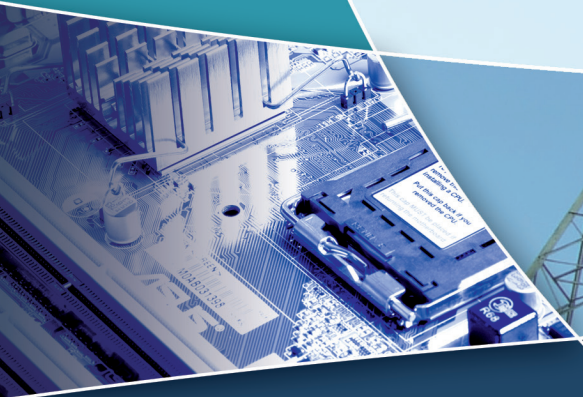




Introduction to electric installations and technology

Juan Pérez Cruz | Manuel Pineda Sánchez
Rubén Puche Panadero | Ángel Sapena Bañó



EDITORIAL
UNIVERSITAT POLITÈCNICA DE VALÈNCIA

Juan Pérez Cruz
Manuel Pineda Sánchez
Rubén Puche Panadero
Ángel Sapena Bañó

Introduction to Electric Installations and Technology

EDITORIAL
UNIVERSITAT POLITÈCNICA DE VALÈNCIA

The publication of this book has been approved by the Department of Electrical Engineering of the Universitat Politècnica de València (Spain)

Academic Book Collection

To cite this publication please use the following reference: PÉREZ CRUZ, J., [et al] (2016). Introduction to Electric Installations and Technology. Valencia: Universitat Politècnica de València

Primera edición, 2016 (versión impresa)
Primera edición, 2016 (versión electrónica)

© Juan Pérez Cruz
Manuel Pineda Sánchez
Rubén Puche Panadero
Ángel Sapena Bañó

Translation by: Marina Pérez Vázquez

© 2016, Editorial Universitat Politècnica de València
Distribution: Tel. +34 - 963 877 012 / www.lalibreria.upv.es / Ref.: 6339_01_01_01

ISBN: 978-84-9048-526-2 (versión impresa)
ISBN: 978-84-9048-527-9 (versión electrónica)

Any unauthorized copying, distribution, marketing, editing, and in general any other exploitation, for whatever reason, of this piece of work or any part thereof, is strictly prohibited without the authors' expressed and written permission.

Prologue

This work was created with the idea to assist and review of certain matters of Electrical Engineering and Electricity. It is intended as a help to students who have to take courses on electrical technology, and as an introduction to the basic applications of single-phase and three-phase circuits.

It is especially aimed to two types of readers: students who access the Electrical Technology course, taught in the Master's Degree in Industrial Engineering, coming from Bachelor Degrees where they have seen very few concepts of electricity. And secondly for those technicians who are new to the field of electrical installations.

This text consists of five units. The first one is about the review of the association of passive elements; this unit is very basic, yet essential to understand how you should solve the problems with the various electrical circuits presented in the course. The second unit is about the introduction of single-phase circuits that serve as the basis for understanding the later three-phase circuits, which are introduced in unit three. The fourth and fifth units are about the approach to the different forms of electrical energy distribution, in both single-phase (unit 4) and three-phase networks (unit 5). All approaches are based on alternating current distributions. There is also an annex where some exercises in previous units are solved.

In order to be as clarifying as possible, we have developed a large number of examples. They always refer to the closest environment, many figures have been used, and the most important concepts have been repeated many times.

A bibliography has been included with two types of texts; the most basic type (*) complementary to this text and others that are an extension and application (**) of what is studied in this text.

Finally, we want to thank the colleagues of the Teaching Unit to which we belong and especially Mr José Roger for the support and help given in the preparation of this text.

Index

Prologue	3
Index	5
Unit 1 Association of Passive Elements	9
1.1. Association of passive elements. Resistances	9
1.2. Association of passive elements. Inductors	14
1.3. Association of passive elements. Capacitors	20
1.4. Association of different passive circuit elements	26
1.5. R-L circuit	27
1.6. R-C circuit	29
1.7. L-C circuit	30
1.8. R-L-C circuits	33
Unit 2 Single-phase Electrical Installations	37
2.1. Parameters in a single-phase electrical installation	37
2.2. Relation between the electrical magnitudes	40

2.2.1.	Relation between voltage (U) and the current (I). Impedance (\bar{Z})	40
2.2.2.	Relation between voltage (U) and current (I). Power (S, P and Q)	43
2.3.	Energy losses and voltage drops	44
2.4.	Approach and solving exercises	53
2.5.	Proposed exercises	58
Unit 3	Three-phase AC circuits	61
3.1.	Introduction	61
3.2.	Representation of a balanced three-phase system	62
3.3.	Voltages in a three-phase system	64
3.4.	Power in a three-phase system	73
3.5.	Energy losses and voltage drops in a three-phase system	78
3.6.	Star and Delta connections	82
3.7.	Connection of the terminal board in a motor	87
Unit 4	Usual applications of single-phase installations	93
4.1.	Electrical installations in housing	94
4.2.	Protection and sections of the lines in housing	95
4.2.1.	Representation and diagrams of the usual circuits in electrical installations in housing	96
4.2.2.	Representation and diagrams of other less common circuits in electrical installations in housing	100
4.2.3.	Representation and diagram of the overall circuits in housing	102
4.3.	Single-phase installations for small businesses and other services	103
4.4.	Guide to determine the section of the conductors	105
4.5.	Other single-phase installations	107
Unit 5	Typical applications of industrial three-phase installations	109
5.1.	Three-phase electrical installations for energy distribution within the industry premises	110
5.1.1.	Three-phase electrical installations in the energy distribution within the industry, using a main distribution line	110
5.1.2.	Three-phase electrical installations in the energy distribution within the industry, using several distribution lines	113

5.2.	Introduction to industrial automation	117
5.2.1.	Automating the startup of a motor with a switch	118
5.2.2.	Automating the startup of a motor through stop and start pushbuttons.....	120
5.2.3.	Automation of a motor that has to operate in the two possible directions of rotation, left and right.....	121
5.2.4.	Automation of a motor start up using a Star-Delta configuration.....	122
Annex 1	127
Bibliography	141

Unit 1

Association of Passive Elements

1.1. Association of passive elements. Resistances

There are two ways to connect the resistances:

- a) Series connection:

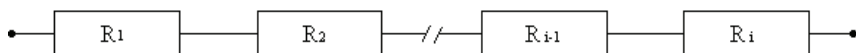


Figure 1.1

The resulting value of the resistance assembly is the sum of them all.

$$R_T = R_1 + R_2 + \dots + R_i$$

Example 1.1.- In the circuit in Figure 1.2 , composed of 3 resistances, whose values are $R_1 = 10 \Omega$, $R_2 = 15 \Omega$ and $R_3 = 27 \Omega$. Calculate the equivalent resistance:

$$R_T = R_1 + R_2 + R_3 = 10 + 15 + 27 = 52 \Omega$$

$$\boxed{R_T = 52 \Omega}$$

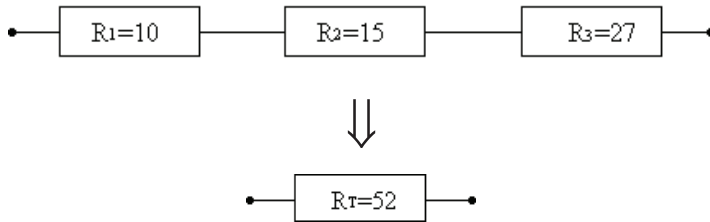


Figure 1.2

b) Parallel connection:

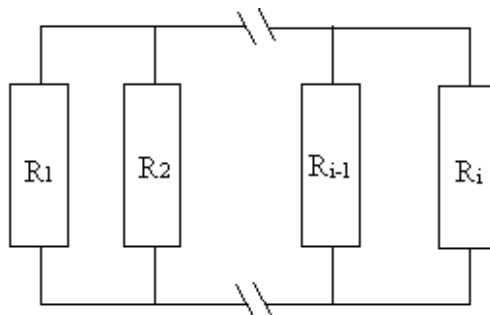


Figure 1.3

The resulting value of the resistance assembly is:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_i}$$

Example 1.2.- In the circuit in Figure 1.4, where there are three parallel resistances whose values are $R_1 = 10 \Omega$, $R_2 = 15 \Omega$ and $R_3 = 27 \Omega$. Calculate the equivalent resistance:

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{15} + \frac{1}{27} = \frac{15 \cdot 27}{10 \cdot 15 \cdot 27} + \frac{10 \cdot 27}{10 \cdot 15 \cdot 27} + \frac{10 \cdot 15}{10 \cdot 15 \cdot 27} = \frac{405 + 270 + 150}{4050}$$

$$\boxed{R_T = 4,91 \Omega}$$

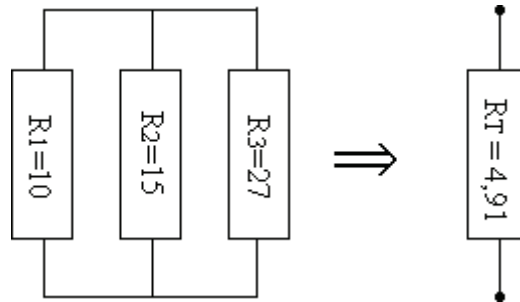


Figure 1.4

- a. In the particular case of 2 resistances in parallel we get the following equation:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \times R_2} \Rightarrow R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

Example 1.3.- In the circuit in Figure 1.5, where there are two parallel resistances whose values are $R_1 = 15 \Omega$ and $R_2 = 27 \Omega$. Calculate the equivalent resistance:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \times R_2} \Rightarrow R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{15 \times 27}{15 + 27} = 9,64 \Omega$$

$$\boxed{R_T = 9,64 \Omega}$$

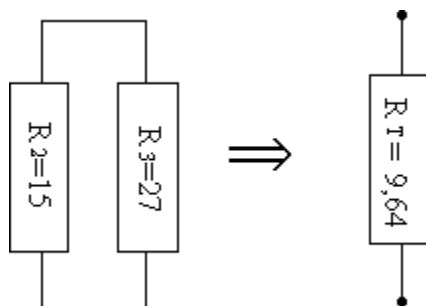


Figure 1.5

b. If the two parallel resistances are equal, we get:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \times R_2} \Rightarrow R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{R^2}{2 \times R} = \frac{R}{2}$$

Example 1.4.- In the circuit in Figure 1.6, where the two resistances are equal and whose value is 27Ω , calculate the equivalent resistance:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \times R_2} \Rightarrow R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{R^2}{2 \times R} = \frac{R}{2} = \frac{27}{2} = 13,5 \Omega$$

$$\boxed{R_T = 13,5 \Omega}$$

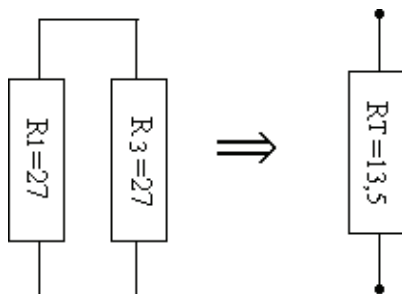


Figure 1.6

Note: For the case of association of series connection of resistances, the resulting resistance value is always higher than the highest of them all, while in the case of parallel connection of resistances the value of the resulting resistance is always lower than the lowest value of the group. If there are 2 equal resistances in parallel connection the result value is half of the associated resistance. If there are three equal resistances in parallel connection the resultant value of the resistance is $R/3$, etc.

c) Series parallel connection of resistances:

It is solved similarly to the previous cases. Initially gathering the resistances in parallel, we obtain a unique value for each group of resistances in parallel, as it has been done in section (b). This way we get a circuit with only resistances in series, which is now solved as it has been done in section (a).

Example 1.5.- In the circuit in Figure 1.7, there are two groups of parallel resistances: one with 2 resistances with values $R=20\ \Omega$ and $R=25\ \Omega$, another parallel circuit with resistances with values $R=10\ \Omega$ and $R=17\ \Omega$, and another resistance in series with value $R=40\ \Omega$. Calculate the equivalent resistance.

$$R_{p1} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 25}{20 + 25} = 11,11\ \Omega \quad R_{p2} = \frac{R_3 \times R_4}{R_3 + R_4} = \frac{10 \times 17}{10 + 17} = 6,30\ \Omega$$

$$R_T = R_{p1} + R_{p2} + R_5 = 11,11\ \Omega + 6,30\ \Omega + 40\ \Omega = 57,41\ \Omega$$

$$\boxed{R_T = 57,41\ \Omega}$$

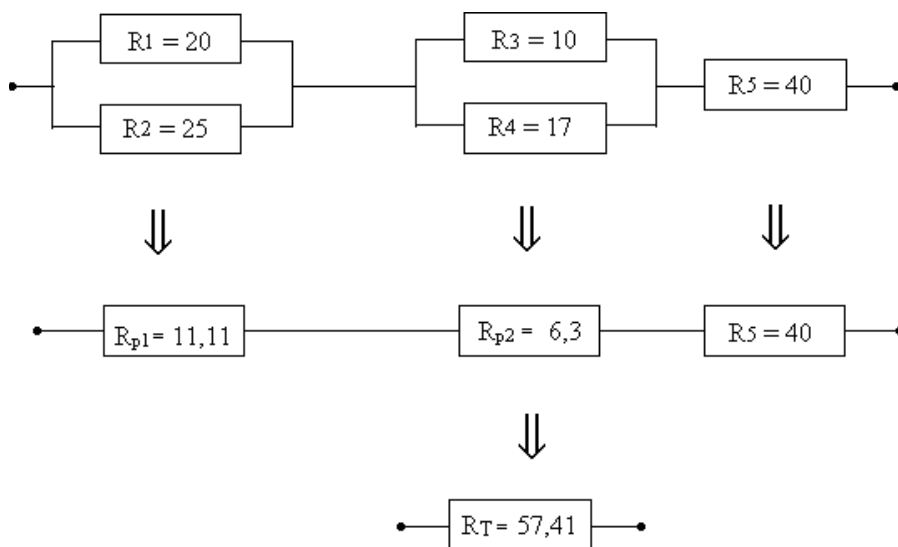


Figure 1.7

1.2. Association of passive elements. Inductors

In circuits where only inductors appear, the association between them is performed similarly to the case of the resistances. The value of the inductance (L) of an inductor is expressed in henries, although due to the small size of the usual values they usually come expressed in milli-henries (mH):

- a) Association of inductors in series. The inductance value of the resulting inductor is the sum of the values of the circuit series inductances.

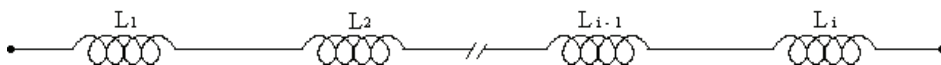


Figure 1.8

$$L_T = L_1 + L_2 + \dots + L_i$$

Example 1.6.- In the circuit in Figure 1.9, where $L_1 = 10$ mH, $L_2 = 15$ mH, and $L_3 = 27$ mH, calculate the equivalent inductor.

Para seguir leyendo haga click aquí